

Digital Systems

Physics 5430

Chapter 3 Part 1 – Busses,
Multiplexing ASM Inputs

Bus Notation

TYPO: ROM has MSB of address and data pins at the top. **Always put LSB at top.**


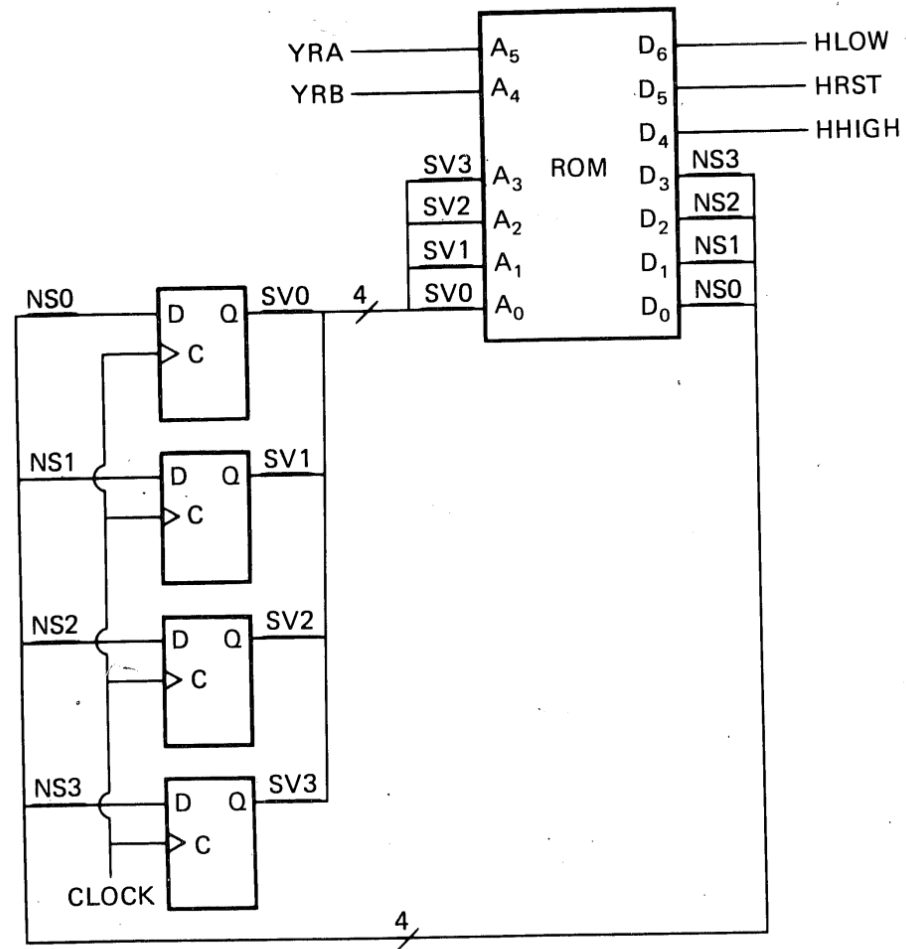


Figure 3-1 Notation for bus.

Showing all the signal lines clutters the schematic. Instead, use a single line for bus, split out the inputs and outputs at the ends of the bus. Label bus with number of signal wires, e.g., use /4.

Bi-directional Data Bus

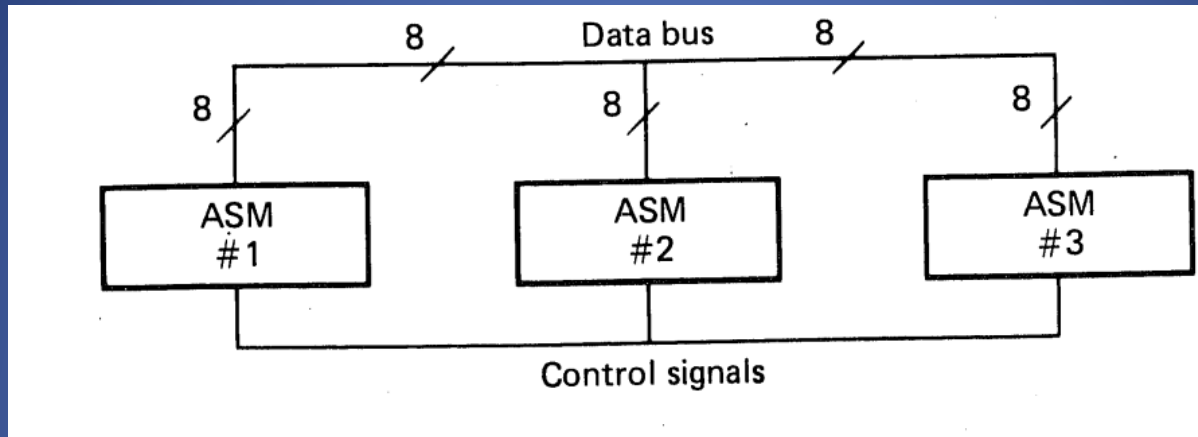

Data is passed between 3 ASMs.


Control signals specify which ASM is the transmitter.

All three ASMs are simultaneous receivers.

Two popular methods are:

- 1) Wired-AND (used in the IEEE-488 GPIB bus and the I²C bus)
- 2) Tristates

Wired-And Data Bus

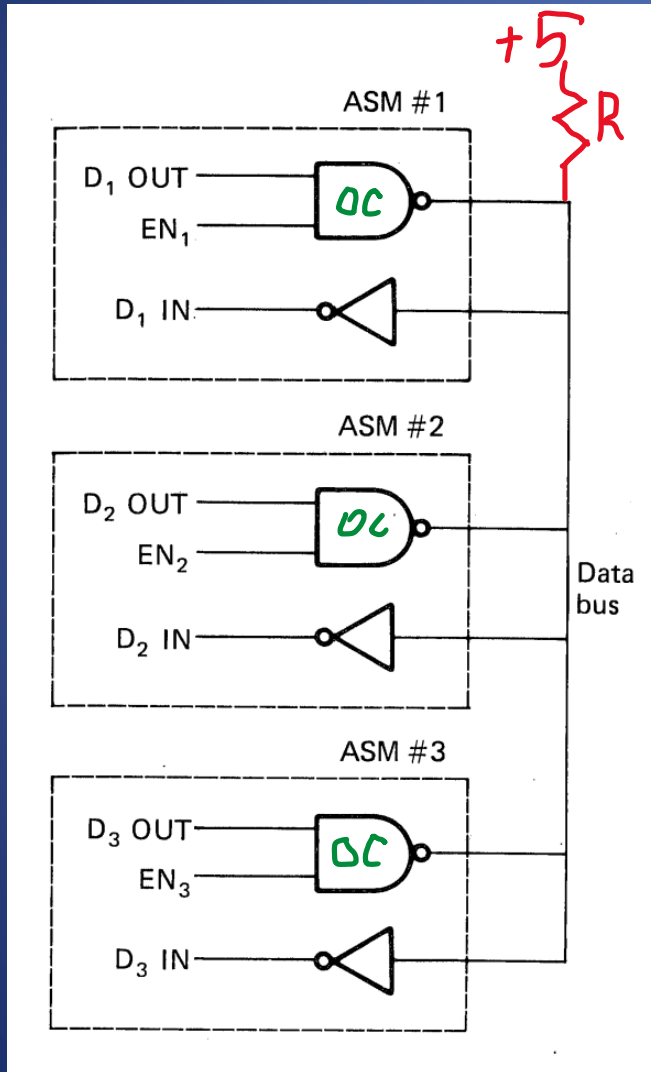

All inputs (e.g., D1 In) are connected to the bus through inverter/buffers.

Only one output is gated onto the bus at a time. An enable signal (e.g., EN1) is applied to the OC NAND gate.

Wired-AND Data Bus (continued)

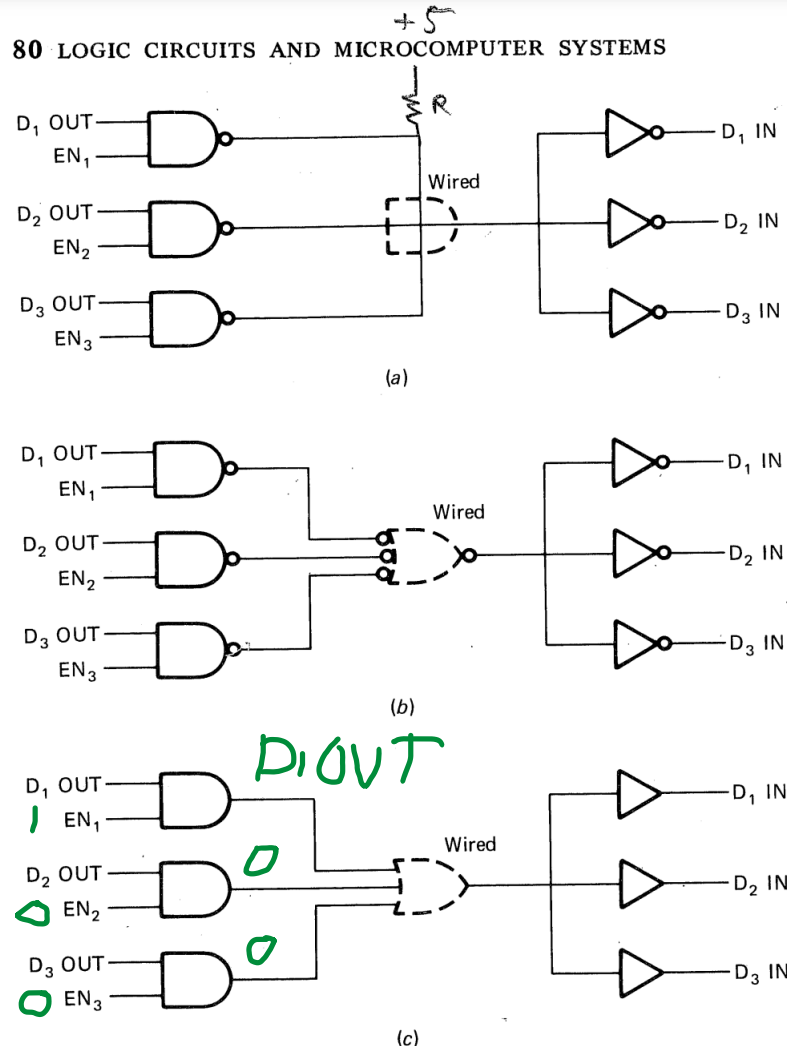


Figure 3-4 (a) Wired AND. (b) De Morgan's law. (c) Equivalent circuit.

Redraw Circuit with Inputs and Outputs grouped

DeMorgan's Law

Equivalent Circuit

Wired-AND Data Bus (continued)


Wired-AND data bus ends up with transmitters Ored to receivers. Each transmitter can put its data on the bus if it is enabled.

Disadvantage is slower propagation of signal through the gates.

Tristate Bus

Faster signal propagation than Wired-AND bus.

Tristate Inverter

 

is
equivalent
to


 


Figure 3-5 Inverter with three-state output.

Tristate Bus

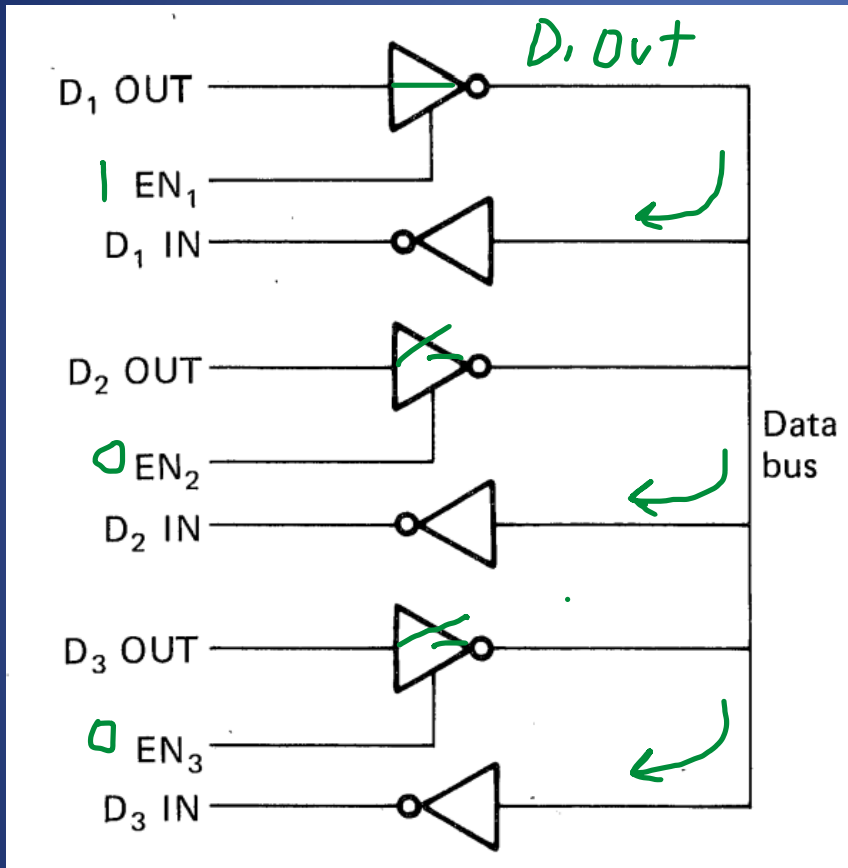

With Enables set to (1,0,0),
D₁ OUT is connected to the
bus.

D₂ OUT and D₃ OUT are
disconnected from the bus.

Note: This circuit of inverters provides the same
functionality as the previous Wired- AND bus.

Scale of Integrated Circuits

Standard circuits and algorithms are used repeatedly in digital electronics. These are MASS PRODUCED which (1)Lowers production costs, and (2)Lowers DESIGN costs, since the cost is shared by millions of IC's.

Chips are categorized according to complexity (the number of gates per chip).

SSI (Small Scale Integration) 1-20 gates per chip.

MSI (Medium Scale Integration) 20-100 gates/chip.

LSI (Large Scale Integration) 100-1000 gates/chip.

VLSI (Very Large Scale Integration) >1000 gates/chip.


Generally, TTL is used for SSI and MSI. CMOS is used for LSI and VLSI. CMOS is simpler, with a smaller area, and low power.

CMOS Circuits

Complementary Metal Oxide Semiconductor

“Complementary” because the transistors come in n-type and p-type pairs.

What does the following CMOS circuit do?

 

8-7 MOS Technology

 





FIGURE 4.64

Practical Electronics for Inventors
2nd ed. page 169


Enhancement MOSFETs, unlike depletion MOSFETs, have a normally resistive channel; there are few charge carriers within it. If a positive gate-source voltage is applied to an

n-channel enhancement-type MOSFET, electrons within the p-type semiconductor region migrate into the channel and thereby increase the conductance of the channel (see Fig. 4.64c). For a p-channel enhancement MOSFET, a negative gate-source voltage draws holes into the channel to increase the conductivity (see Fig. 4.64d).



CMOS NAND Gate

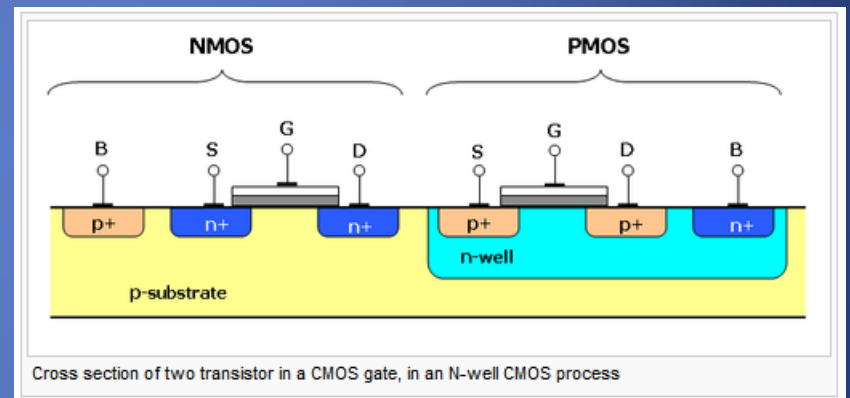 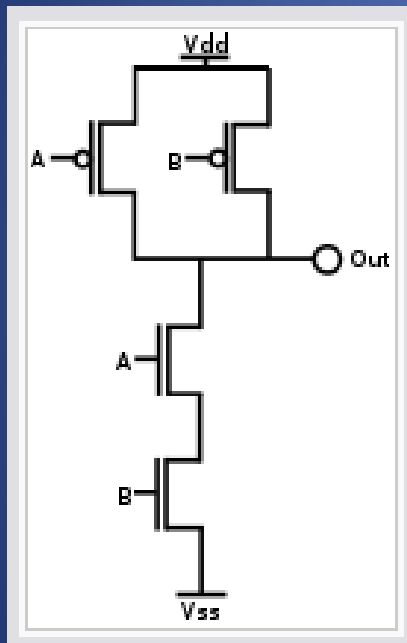


A Simple Multiplexer

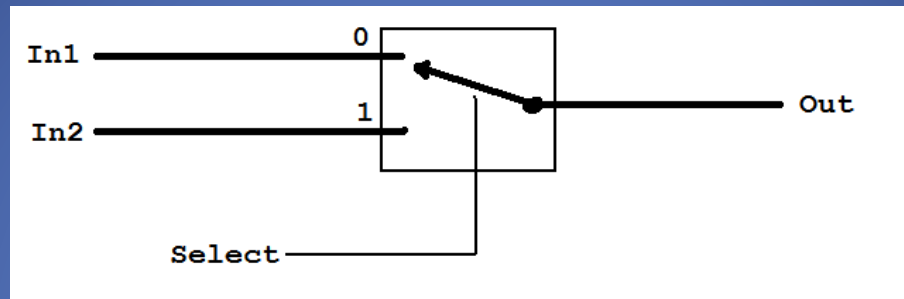

A Simple Multiplexer

  

4 to 1 Multiplexer

 

Select lines BA connect 1 of the 4 inputs to output Y. B is MSB.

W is Y bar.

Strobe is active-low enable.
Y = 0 when disabled.

Table 3-1 Logic table for multiplexer

<i>STROBE</i>	<i>B</i>	<i>A</i>	<i>Y</i>	<i>W</i>
1	X	X	0	1
0	0	0	D ₀	<u>D₀</u>
0	0	1	D ₁	<u>D₁</u>
0	1	0	D ₂	<u>D₂</u>
0	1	1	D ₃	<u>D₃</u>

A = 0, B = 0 selects D0

A = 0, B = 1 selects D1

B = 1, A = 0 selects D2

B = 1, A = 1 selects D3

4 to 1 Multiplexer Internals

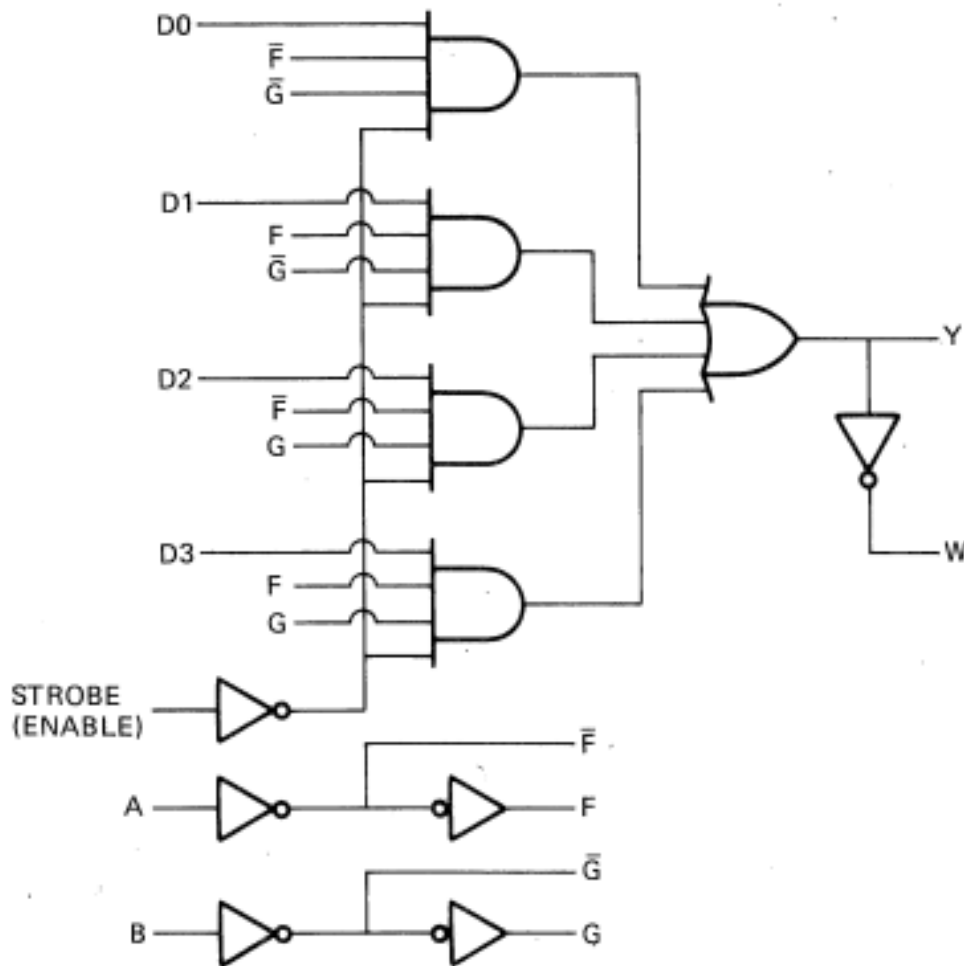


Figure 3-7 4-line to 1-line multiplexer.

Uses four enable gates
(4-input AND gates)

$$F = A, \quad F' = A'$$

$$G = B, \quad G' = B'$$

$F = 0, G = 0$ selects D0

$F = 0, G = 1$ selects D1

$F = 1, G = 0$ selects D2

$F = 1, G = 1$ selects D3

Large Multiplexers

2 to 1, 4 to 1, 8 to 1, and 16 to 1
muxes are commonly available.

Can cascade muxes to make
a larger one.

64 to 1 made from four 16 to 1
cascaded into a 4 to 1.

Has 6 select lines: $2^6 = 64$

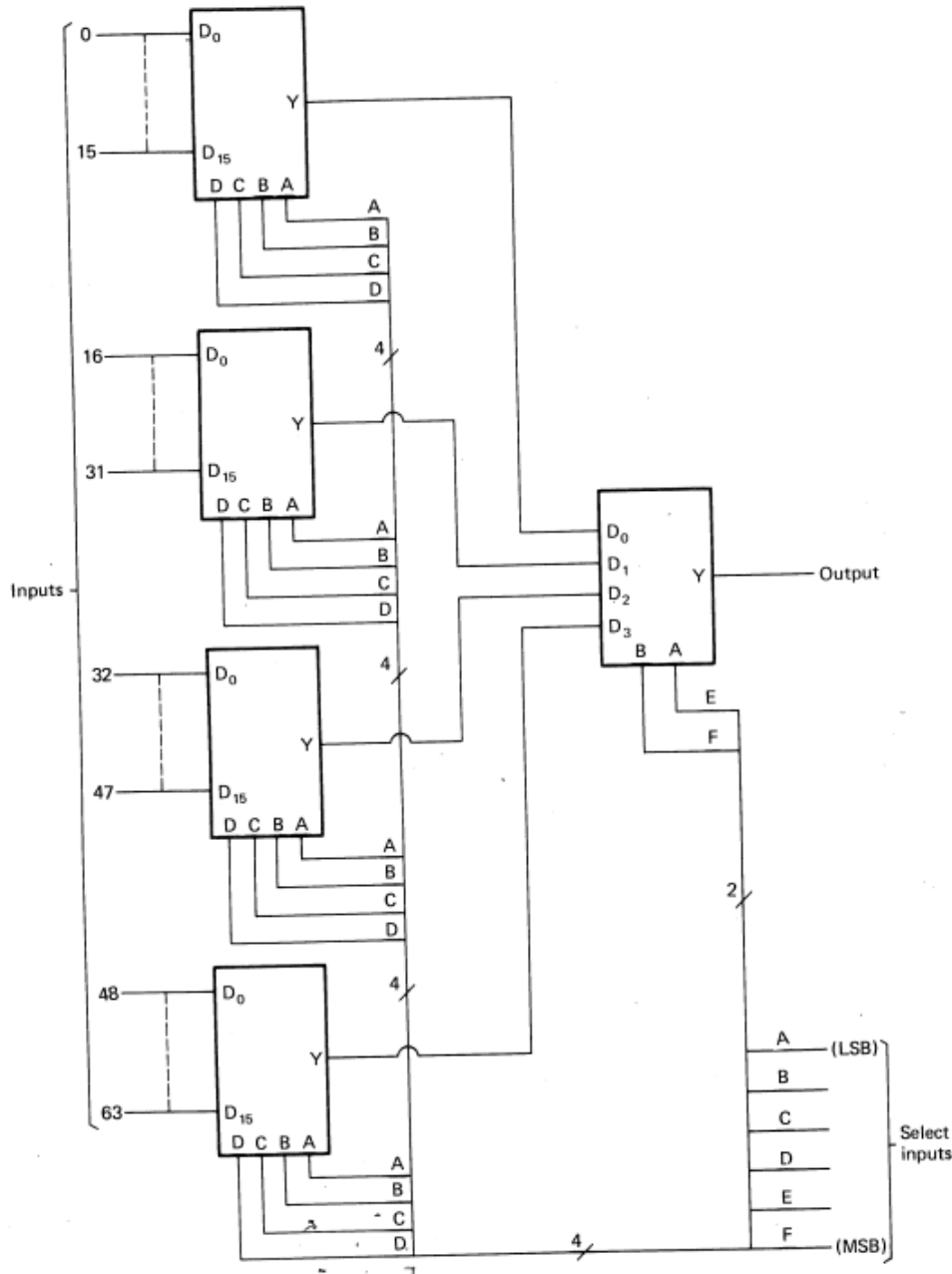


Figure 3-16 Cascading multiplexers.

Using MUX in an ASM

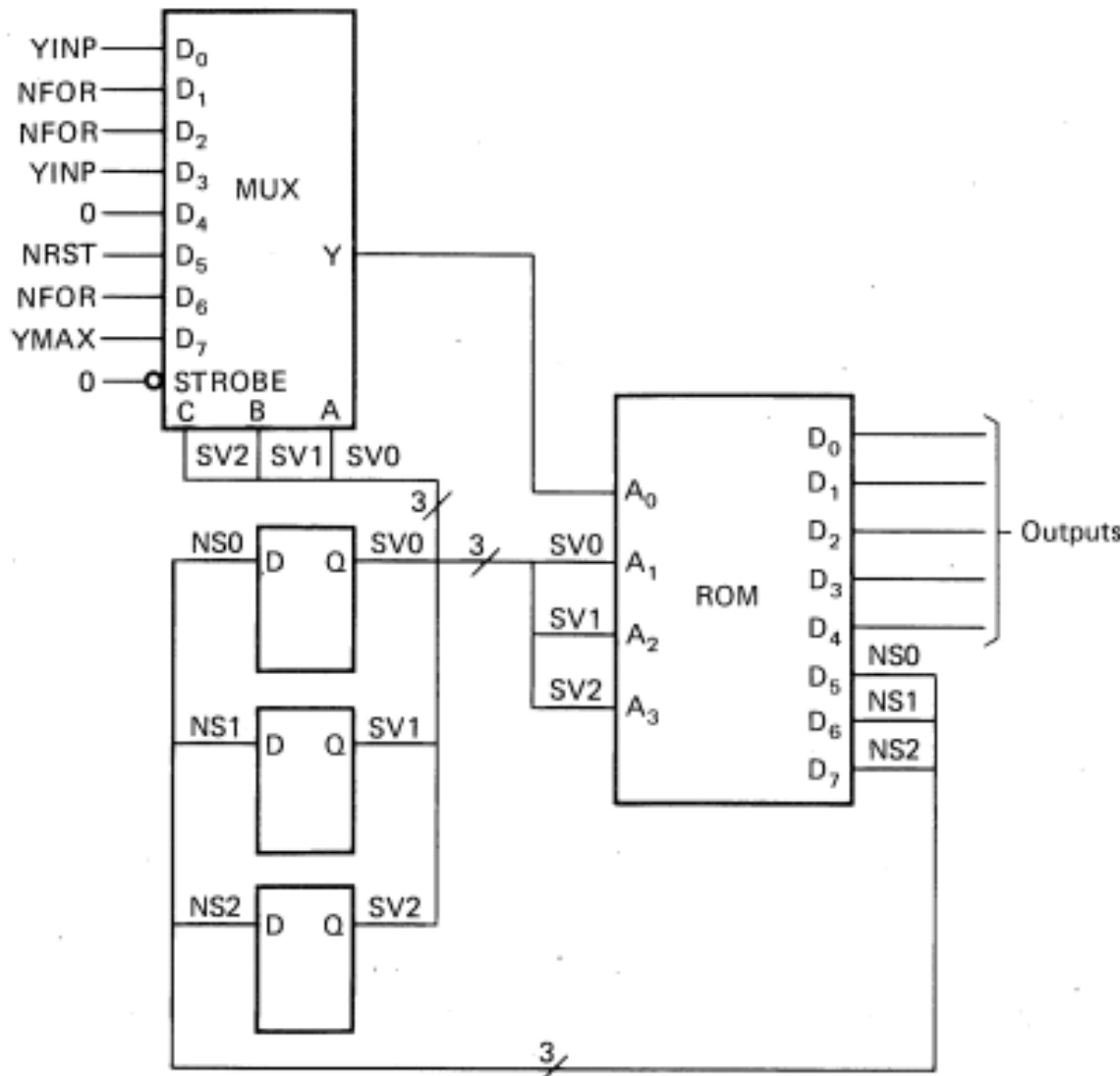


Figure 3-9 Multiplexer for input conditions.

8 to 1 mux connects four ASM inputs into ROM's address pin A0.

Mux select lines CBA tied to state variables.

ONLY 1 input can be tested in each state!

State 0 - YINP

State 1 - NFOR

State 2 - NFOR

State 3 - YINP

State 4 - no input

State 5 - NRST

State 6 - NFOR

State 7 - YMAX

Using MUX in an ASM

ONLY 1 input can be tested in each state (i.e., one decision diamond per state).

Need extra state every time need to test two inputs in same state, **but can't test them at same time.** ASM is also slower (has to step through more states). May need more FFs due to added states.

With mux: 16 x 8 ROM

Testing 2 Inputs at Same Time

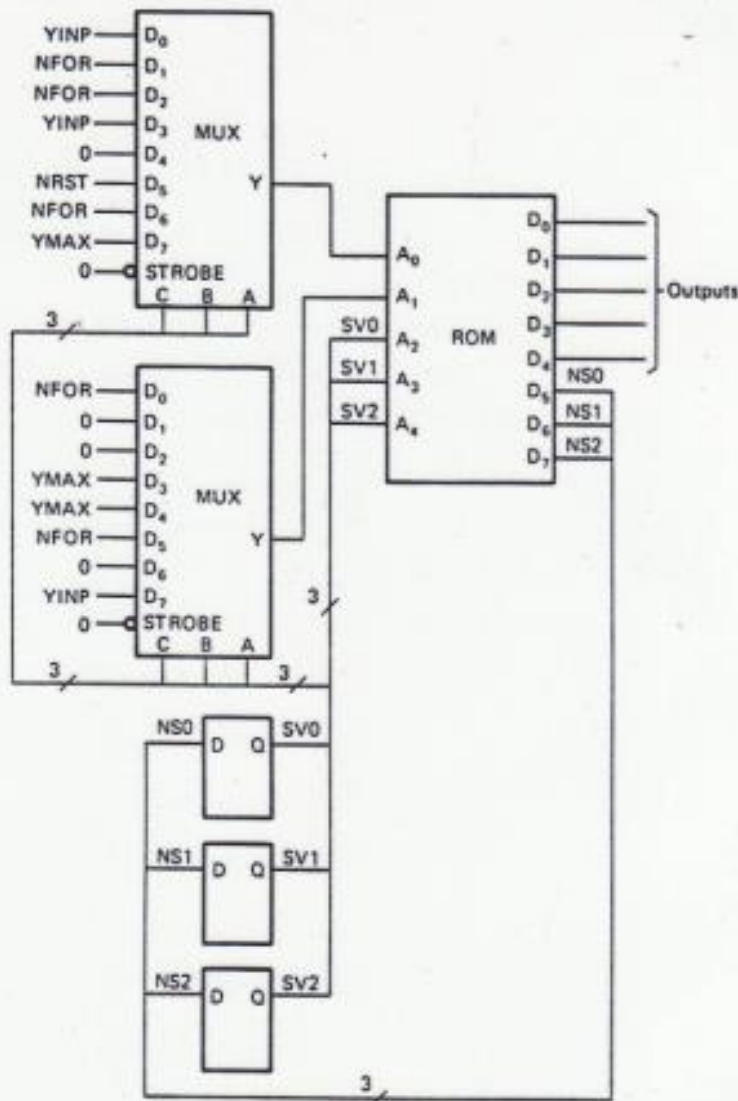


Figure 3-10 Using two multiplexers to test up to two conditions simultaneously.

Use two multiplexers.

Each MUX feeds one address line.
ROM is twice the size (32 x 8).

Smaller than 128 x 8 without muxes.

If have complex ASM – 10 inputs
(2 or 3 tested at the same time)
big savings in ROM size using 2 or 3
muxes.

Assume still has ≤ 8 states (3 FFs).
10 inputs, 3 tested simultaneously:
With muxes: 64 x 8 ROM
Without muxes: 8192 x 8 ROM
Type 8192 lines into ROM table!!!

MUX ASM with Large Number of States

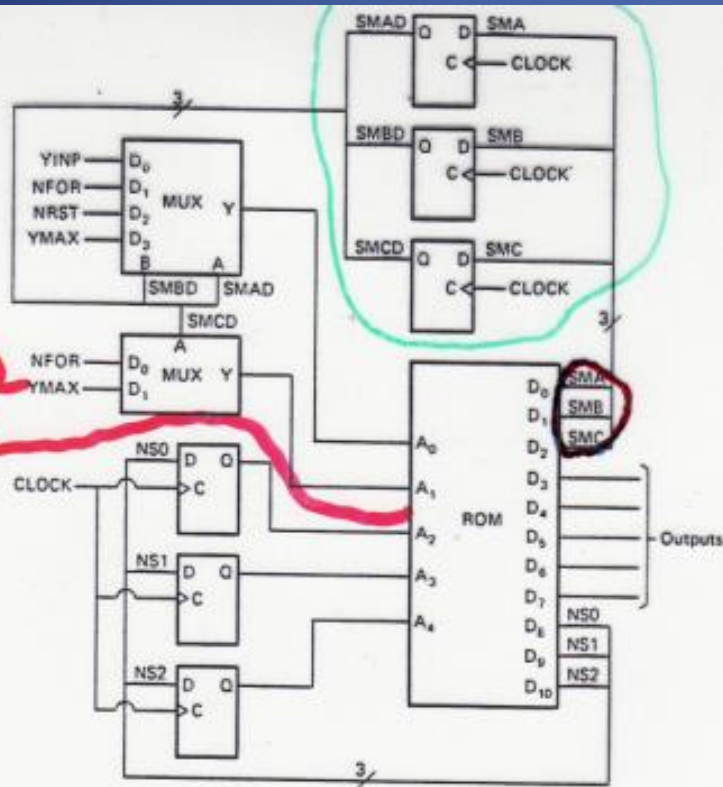


Figure 3-11 Multiplexers controlled by ROM outputs.

If the ASM has 7 state FFs, need $2^7=128$ input MUX! But may only use just a FEW of the 128 inputs.

Therefore, connect MUX select inputs to ROM OUTPUT instead of states. Then the ROM can be programmed to select any input in any state.

Multiple MUX's of different sizes can be used, with some often-used inputs connected directly to the ROM (see the NEMER line [in the figure to the right] that needs to be checked in all states).

NOTE: Need flip-flops in MUX select lines. Why?

MUX ASM with Large Number of States


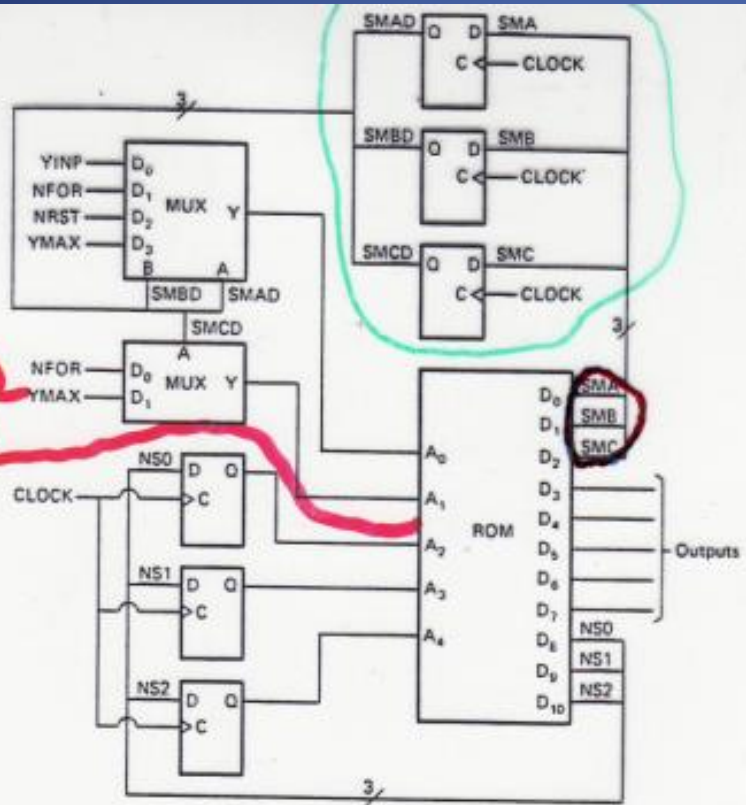


Figure 3-11 Multiplexers controlled by ROM outputs.

NOTE: Need flip-flops in MUX select lines. Why?


ANSWER: The changing input to the ROM could change the outputs of the ROM, changing the select lines, changing the input... Could cause a runaway cycling situation with NO CLOCK needed. FF's synchronize the select lines with the clock. This delays the action of the select line signals one clock pulse, so must be asserted early.

Example Multiplexing ASM Inputs

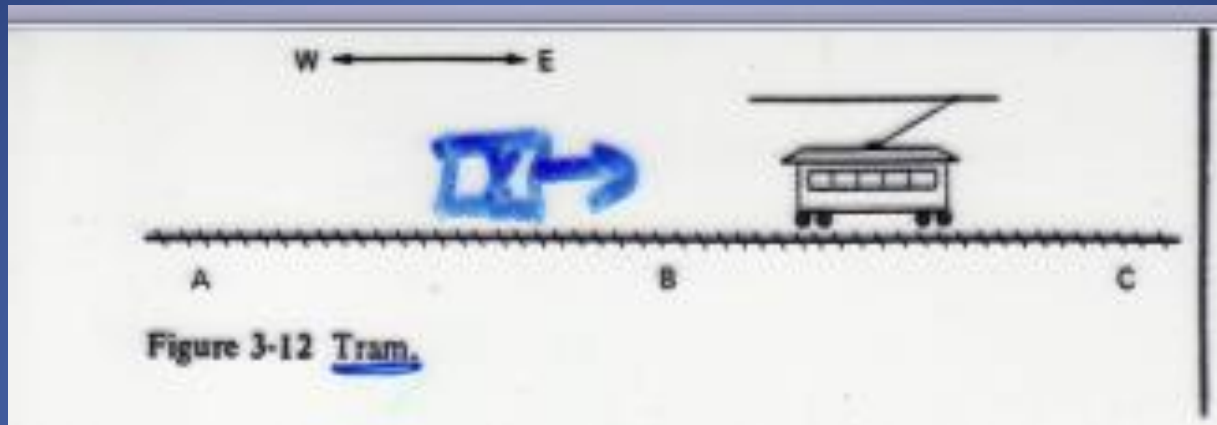

Airport tram car travels between terminals A, B, and C. It must stop within 1 second of actuating sensors at A, B, C; so using 1s clock. It stops 10 seconds (10 states) at each station. Override button keeps it stopped longer at a station as long as conductor is pressing it.

Example Multiplexing ASM Inputs

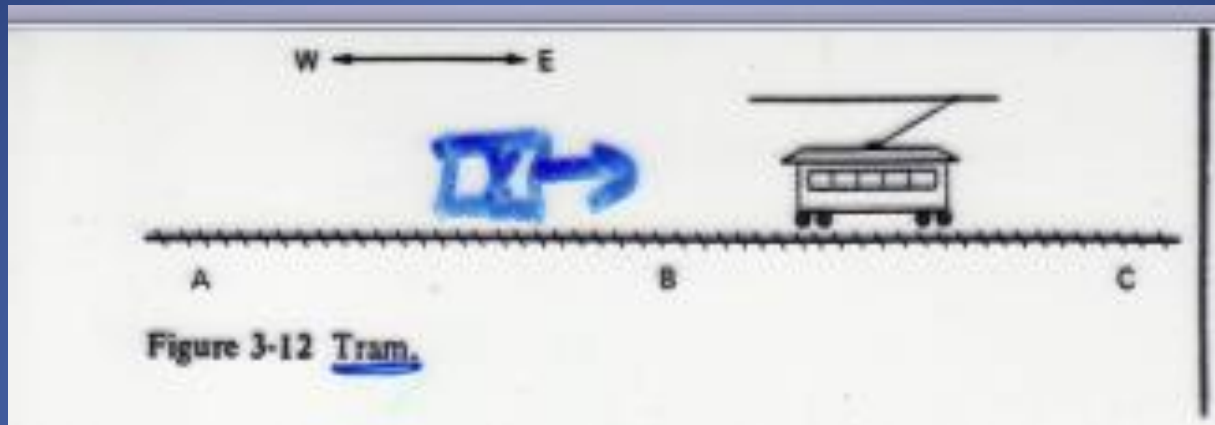

Using a 4-to-1 Mux for inputs A,B,C, and OVERRIDE, so ASM chart tests one input per state. We will have 44 states. That requires 6 FFs and address lines ($2^6=64$), plus one address line for the MUX output. Using ROM outputs for the MUX select lines requires two extra ROM outputs. So we are saving ROM inputs at expense of extra ROM outputs.

Circuit for Tram with MUX

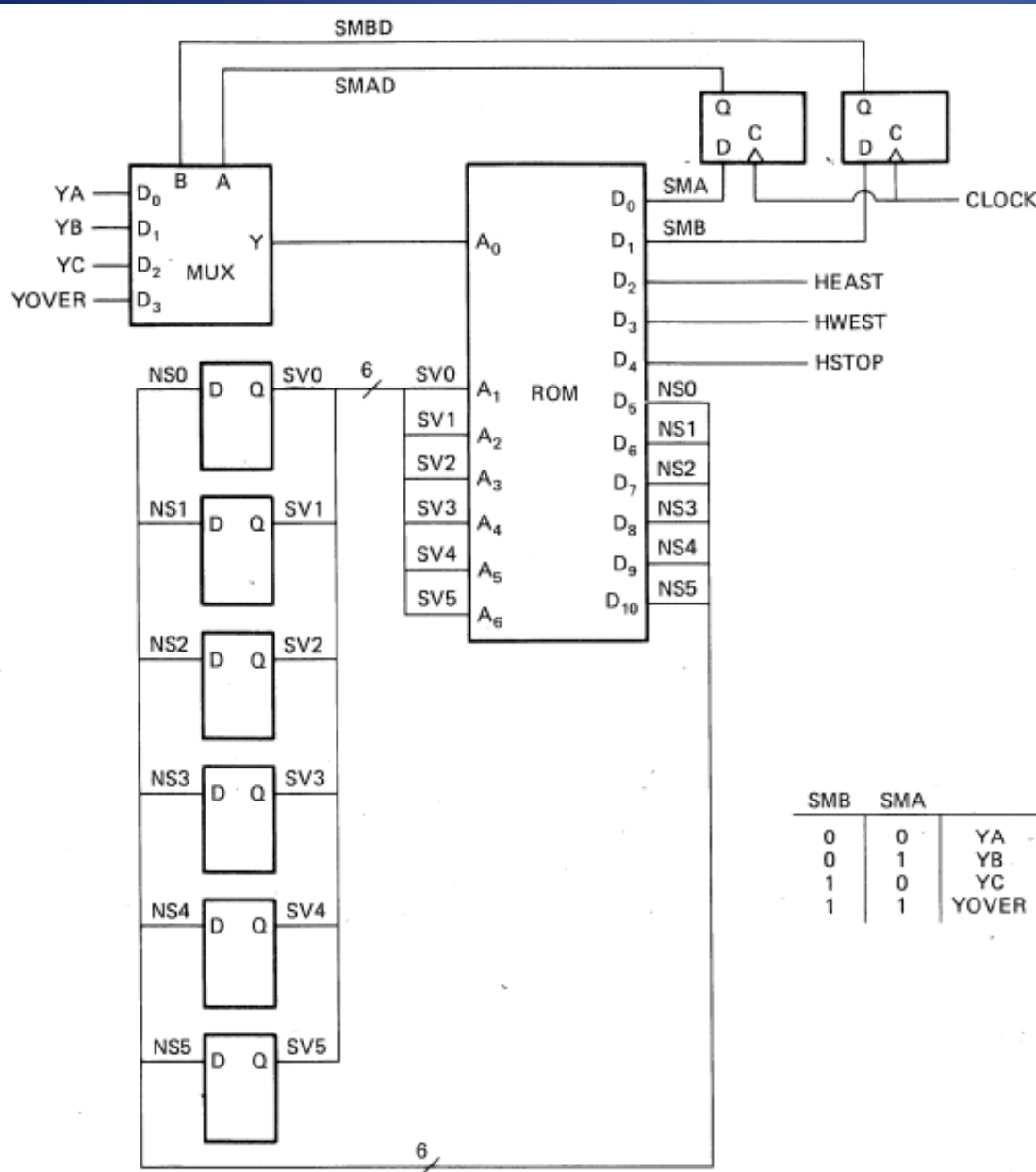


Figure 3-14 Tram controller circuit.

4 to 1 MUX has 2 select lines tied to ROM outputs through FFs.

Notice signal labels:


SMBD =

select mux B delayed

Must activate select lines one state early.

If used state variables for select lines, would need 64 to 1 MUX.

Airport Tram ASM chart

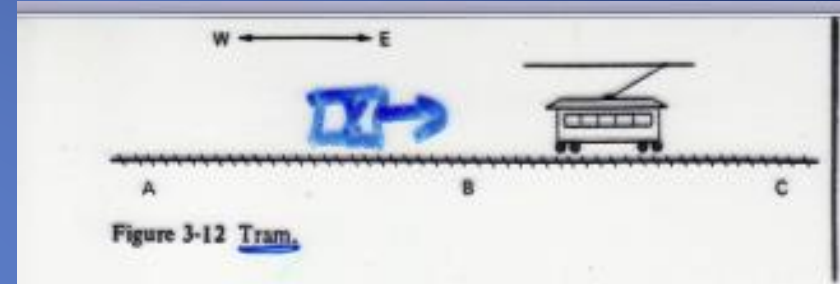

SMB	SMA	
0	0	YA
0	1	YB
1	0	YC
1	1	YOVER

SMB and SMA are asserted
one state early.

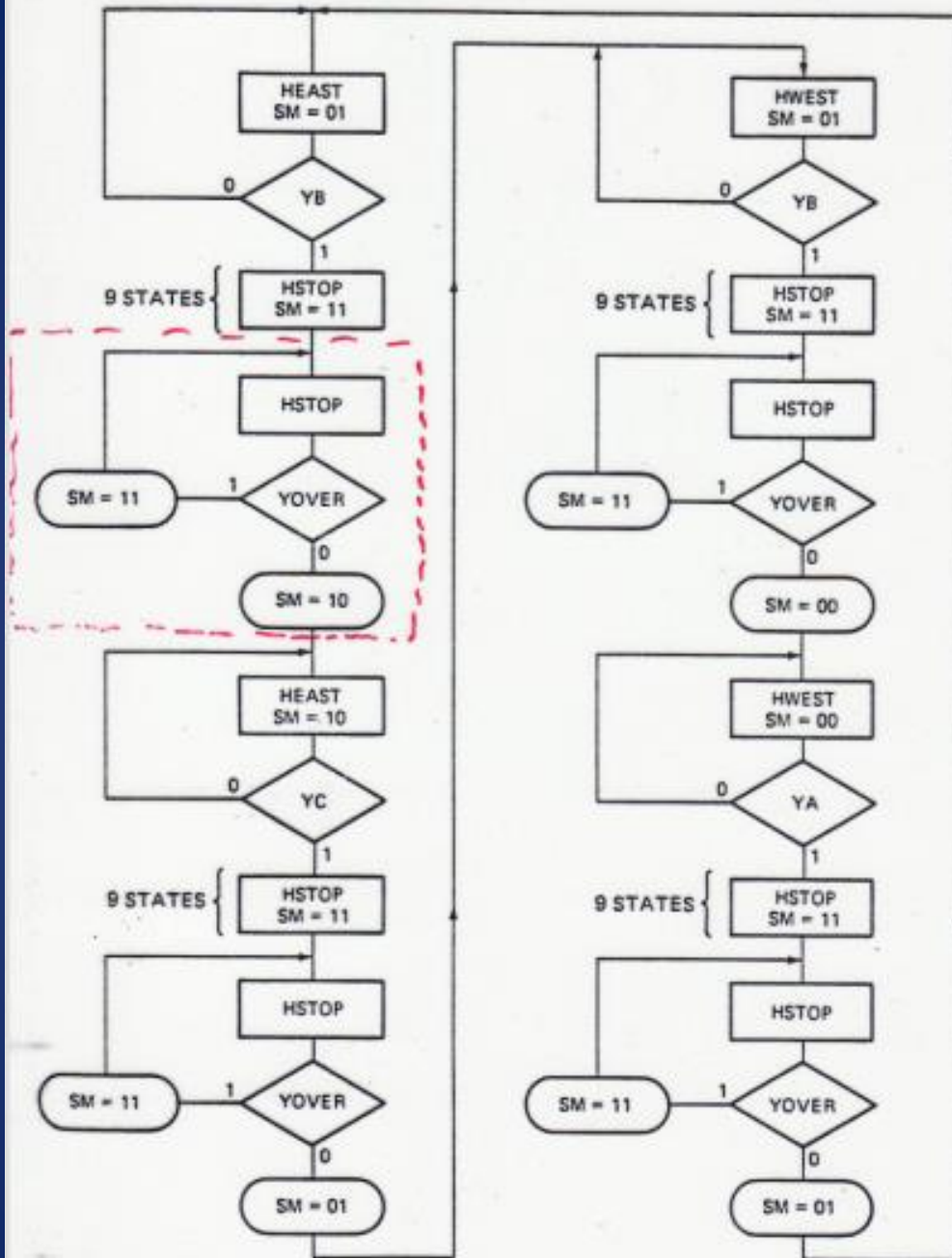


Figure 3-13 ASM chart for tram controller.

Clock = 1 second

Circuit for Tram with MUX

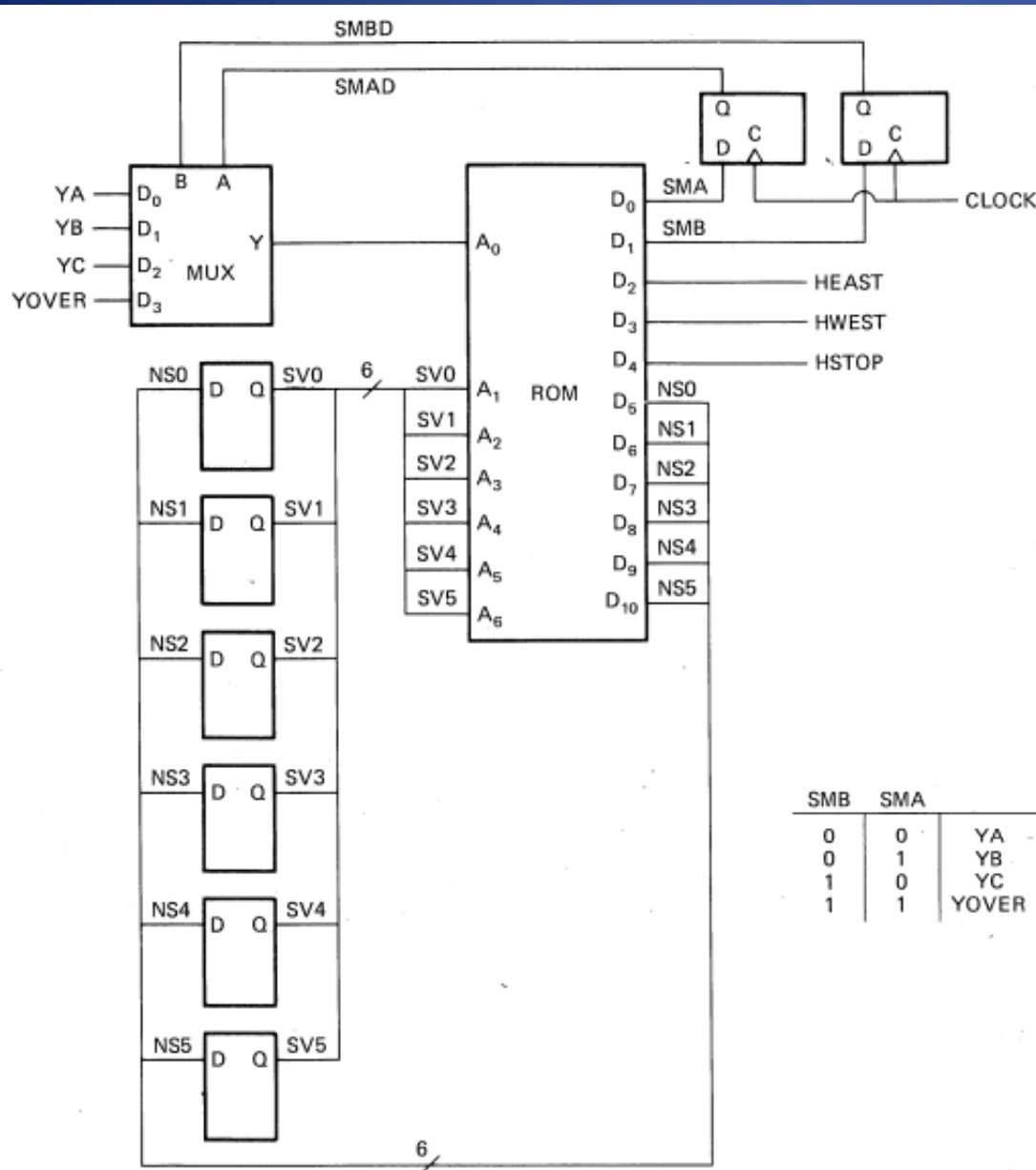


Figure 3-14 Tram controller circuit.

MUX saves 3 address lines,
so ROM is $2^7 = 128 \times 11$

Without mux $2^{10} = 1024 \times 9$

Circuit saves both ROM and
MUX size.

ROM bits

With MUX: $128 \times 11 = 1408$

No MUX: $1024 \times 9 = 9216$

We can use DeCODERS to
lower # ROM outputs to 8.

END