

# Digital Systems

Physics 5430

State Counter and

“The Traffic Light ASM from Hell”

# State Sequencing with Counter

## Replace state reg with state counter.

Counter sequences ASM  
through states in order.

4-bit counter matches 16 States, but we only have 10. So must load counter with 6 every time it tries to roll over to count 0.

Tie active-high CO to active-low LD through an Inverter.


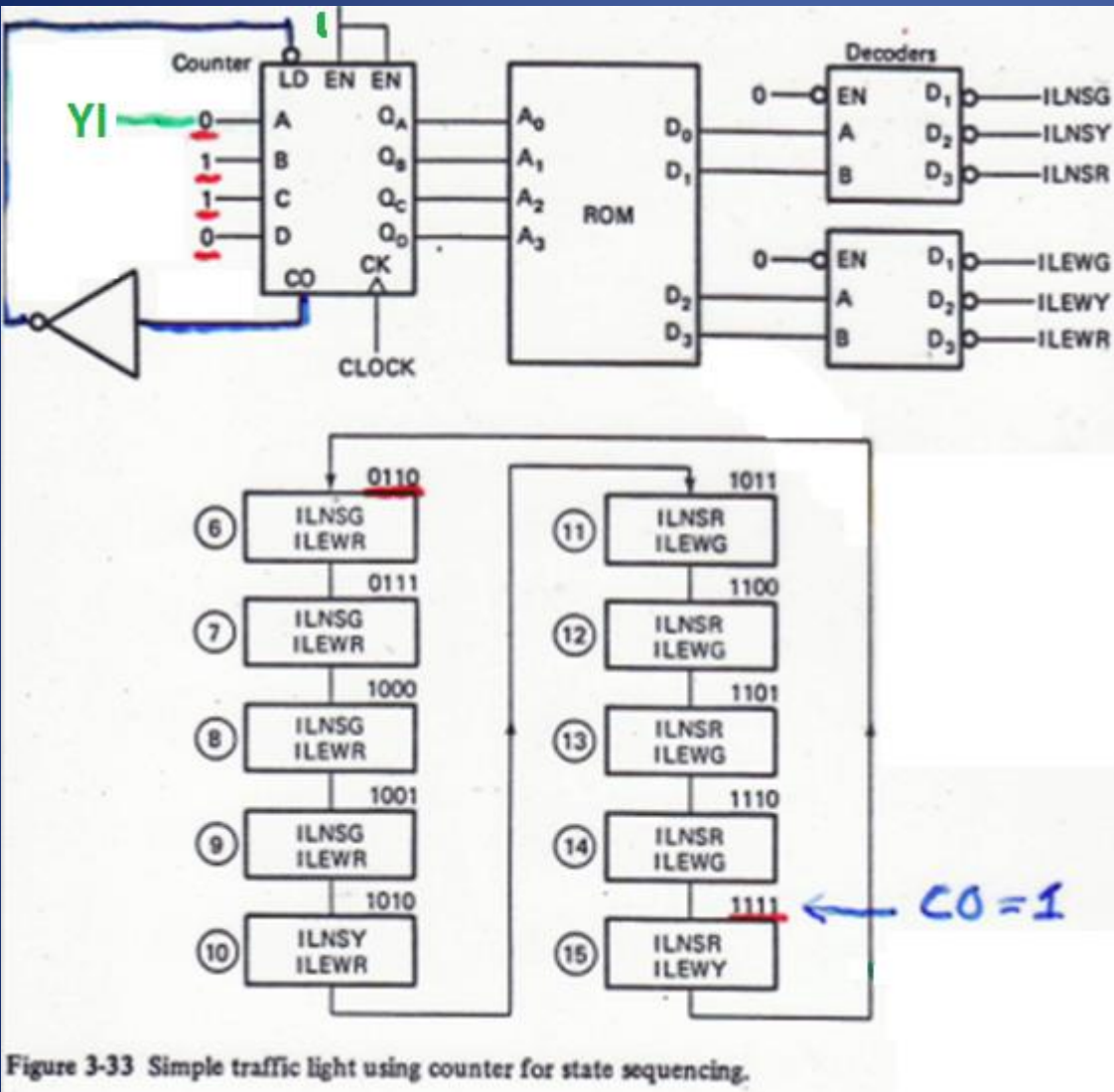


Figure 3-33 Simple traffic light using counter for state sequencing.

**For LIMITED branching (out of state 15 only) to either state 6 or state 7, can connect input Y1 to counter load line A. Or other inputs to other load lines.**

# Flexible Branching with State Counter

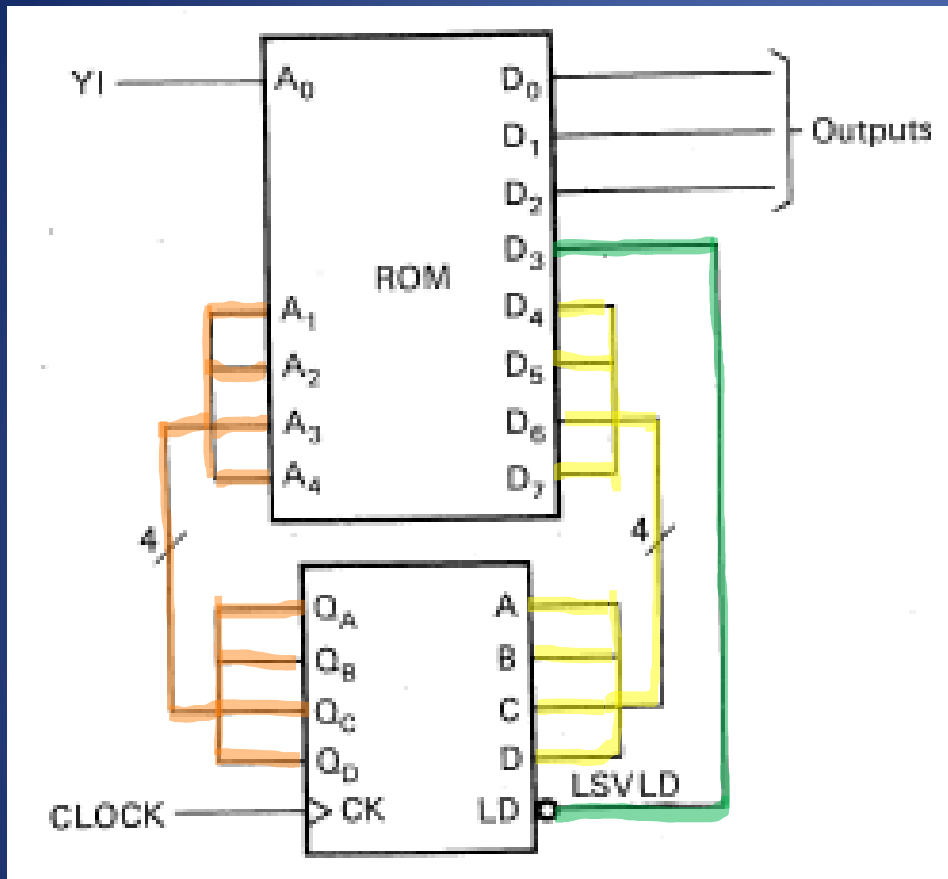

Connect counter outputs to ROM address lines as before.

Connect 4 ROM outputs to the 4 counter inputs.

Connect a ROM output to the counter load pin (LD).

LSVLD is a NEXT STATE output, so acts like delayed output.

**Figure 3-34** Loading an arbitrary next state when using a counter for the state register.

# Flexible Branching ASM Chart

Counter sequences through states 0 to 9.

State 9 has an input YI. If YI = 0, counter keeps sequencing to states 10, 11, 12. In state 12, ROM loads 0 into the counter, so goes to state 0 next.

If YI = 1, ROM loads 14 into the counter, so goes to 14 next. Then counts to 15 and rollover to 0.


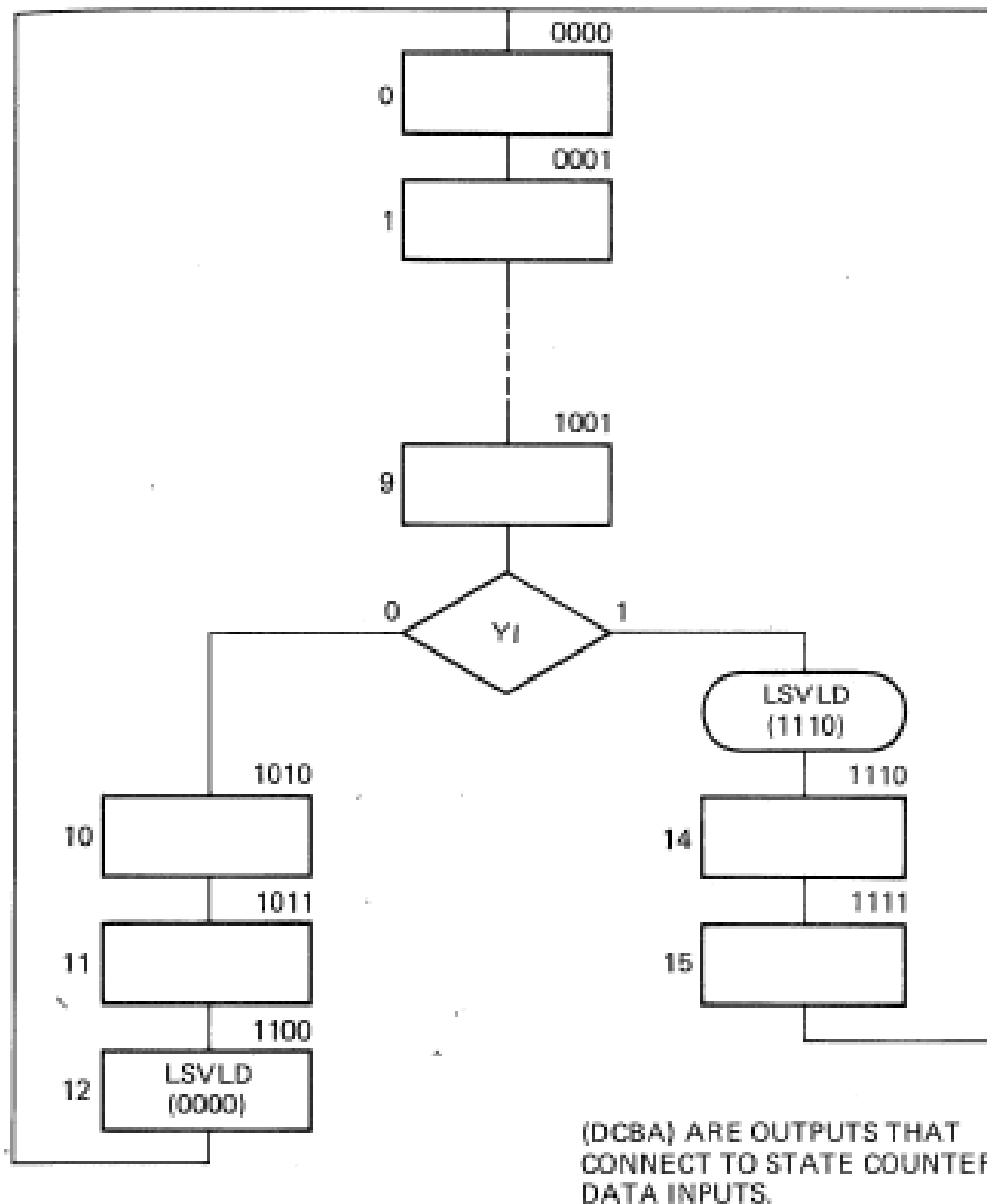


Figure 3-35 ASM chart that loads arbitrary next state into state variable counter.

# Flexible Branching Circuit

 

Using a state counter is much more difficult than a state register.

More importantly, this design uses 5 ROM outputs for the ASM next state instead of 4 without a state counter!


Why would we ever use a state counter?

# Why would we ever use a state counter?

# Answer

It makes sense if you also use the group of 4 state counter ROM outputs for other things. For example, output registers.

You can think of them  
as a data bus.

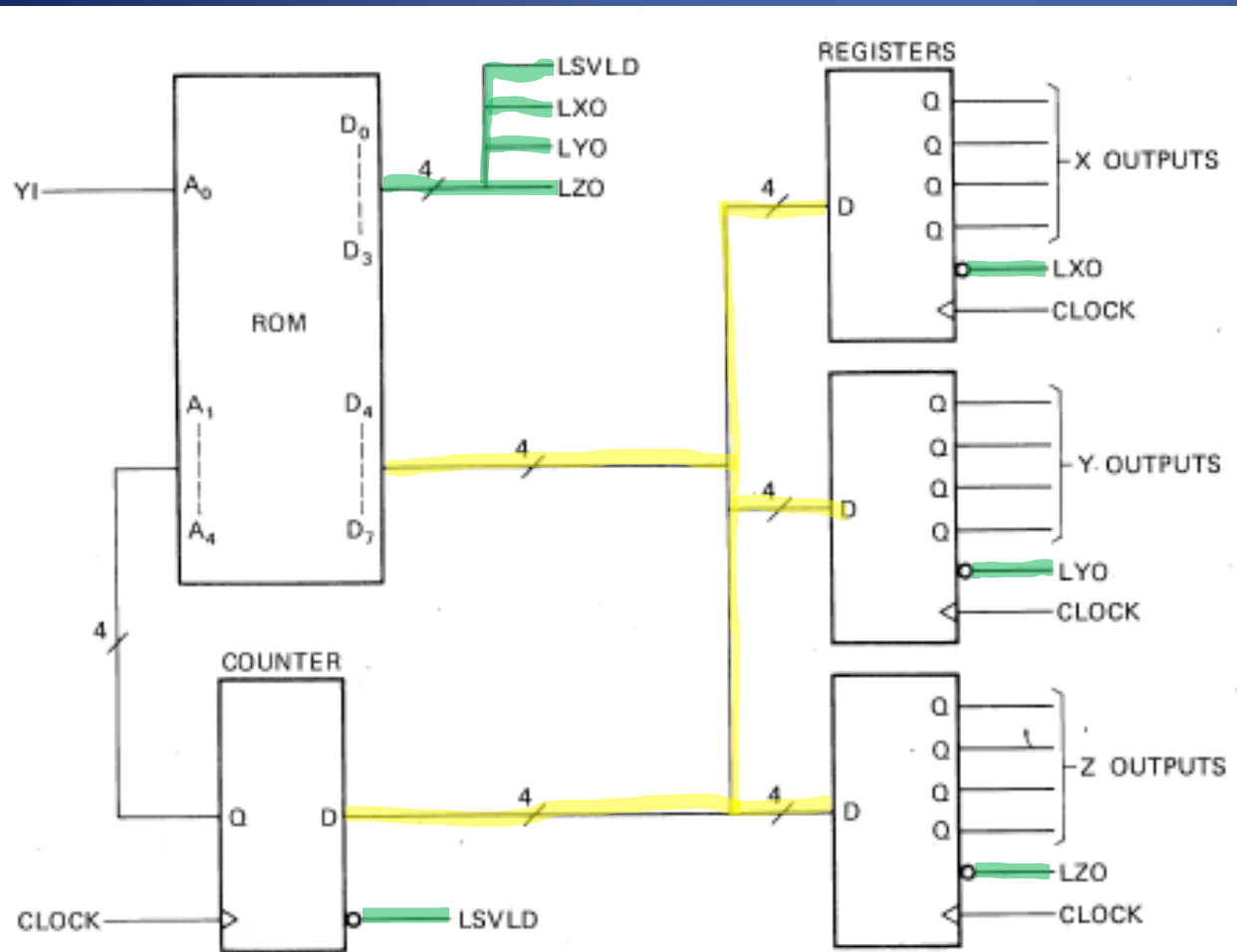

**Figure 3-36** Sharing output and next state ROM outputs.

**LSVLD, LXO, LYO, and LZO are load signals.**



# State Counter with Shared Data Bus

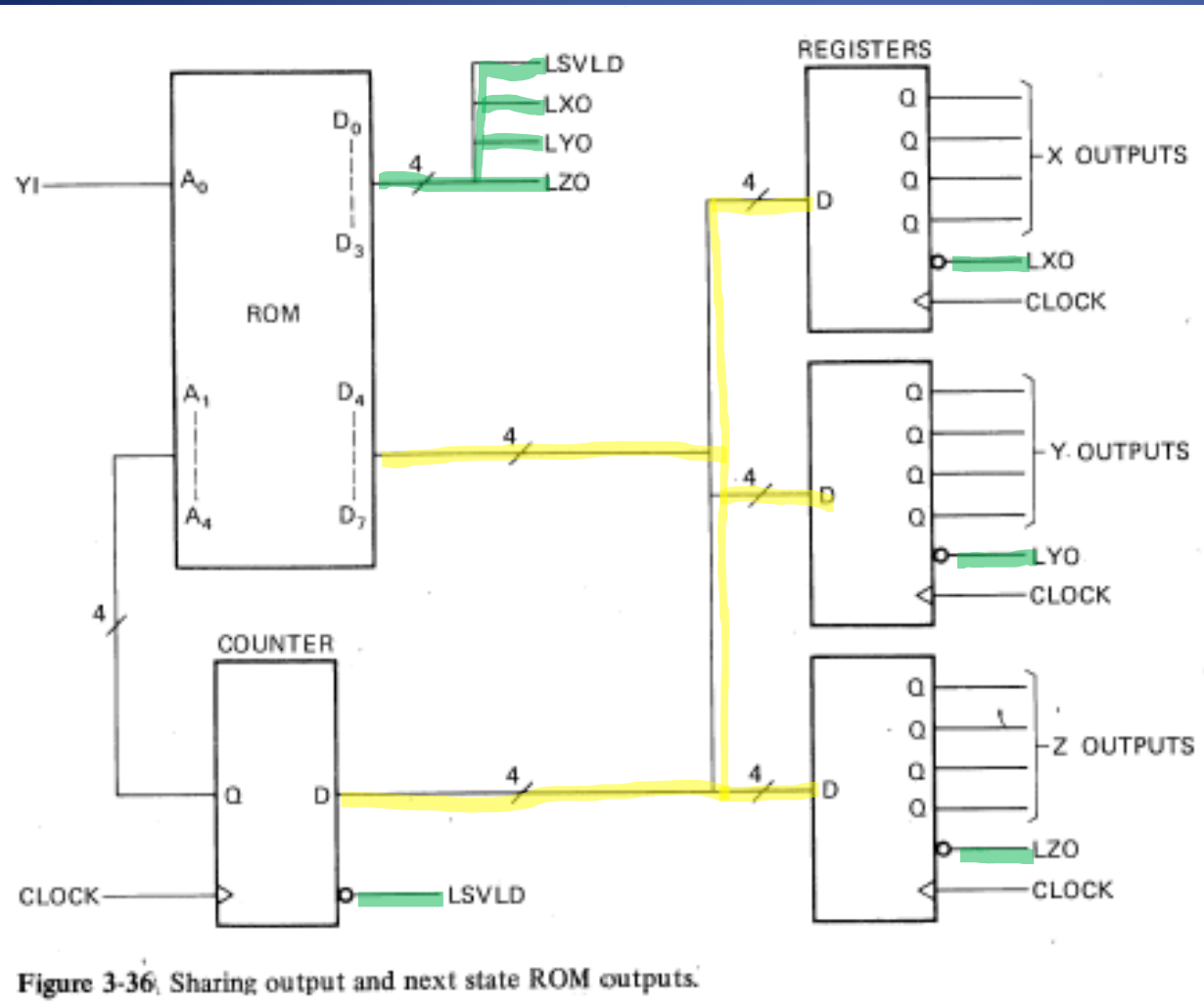


Figure 3-36. Sharing output and next state ROM outputs.

Use data bus and the load signals to load the registers or state counter one at a time.

Requires extra states to load registers.

ASM chart branching may require extra states. (Can't change states and load outputs at same time.)

# State Counter with Shared Data Bus

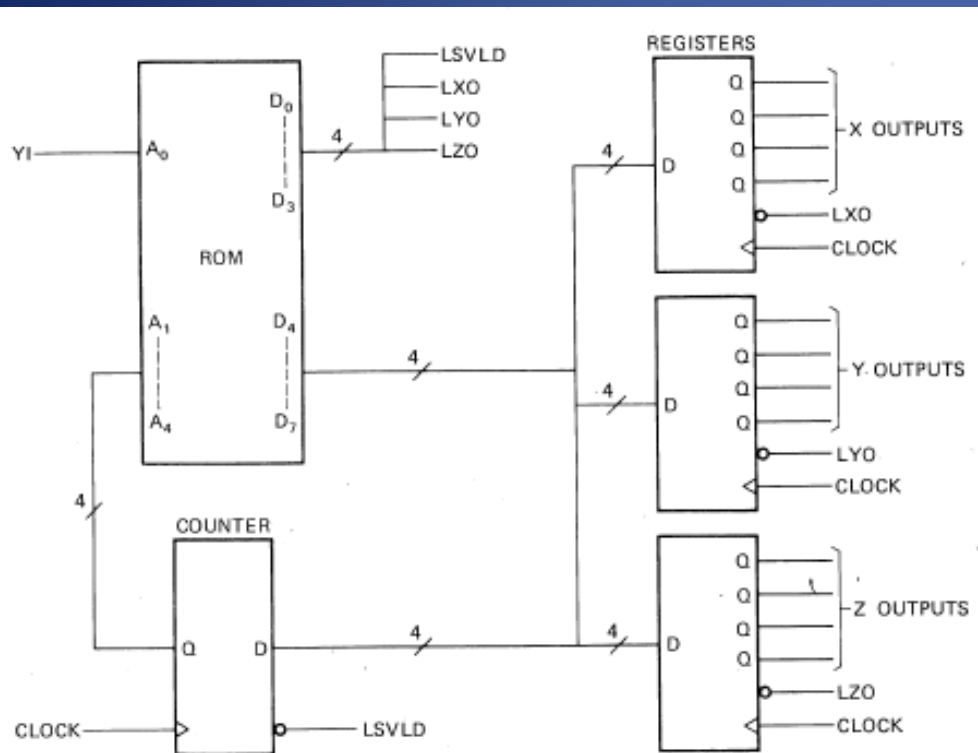


Figure 3-36: Sharing output and next state ROM outputs.

ASM has 8-bit ROM, 12 outputs and up to 16 states.

Standard ASM with 8-bit ROM would only have 4 outputs with up to 16 states.

It would need a 16-bit ROM to have 12 outputs.

How many ROM outputs does the state counter save (not counting the ones the registers save)?

ANSWER: It saves  $4 - 1 = 3$ .

D4-D7 minus LSVLD

How many ROM outputs would using a 1 to 4 decoder for the load signals save?

ANSWER: It saves  $4 - 3 = 1$ , or  $4 - 2 = 2$  if tie EN to gnd. But don't need to save any more (8-bit ROM)



# “Traffic Light ASM from Hell”

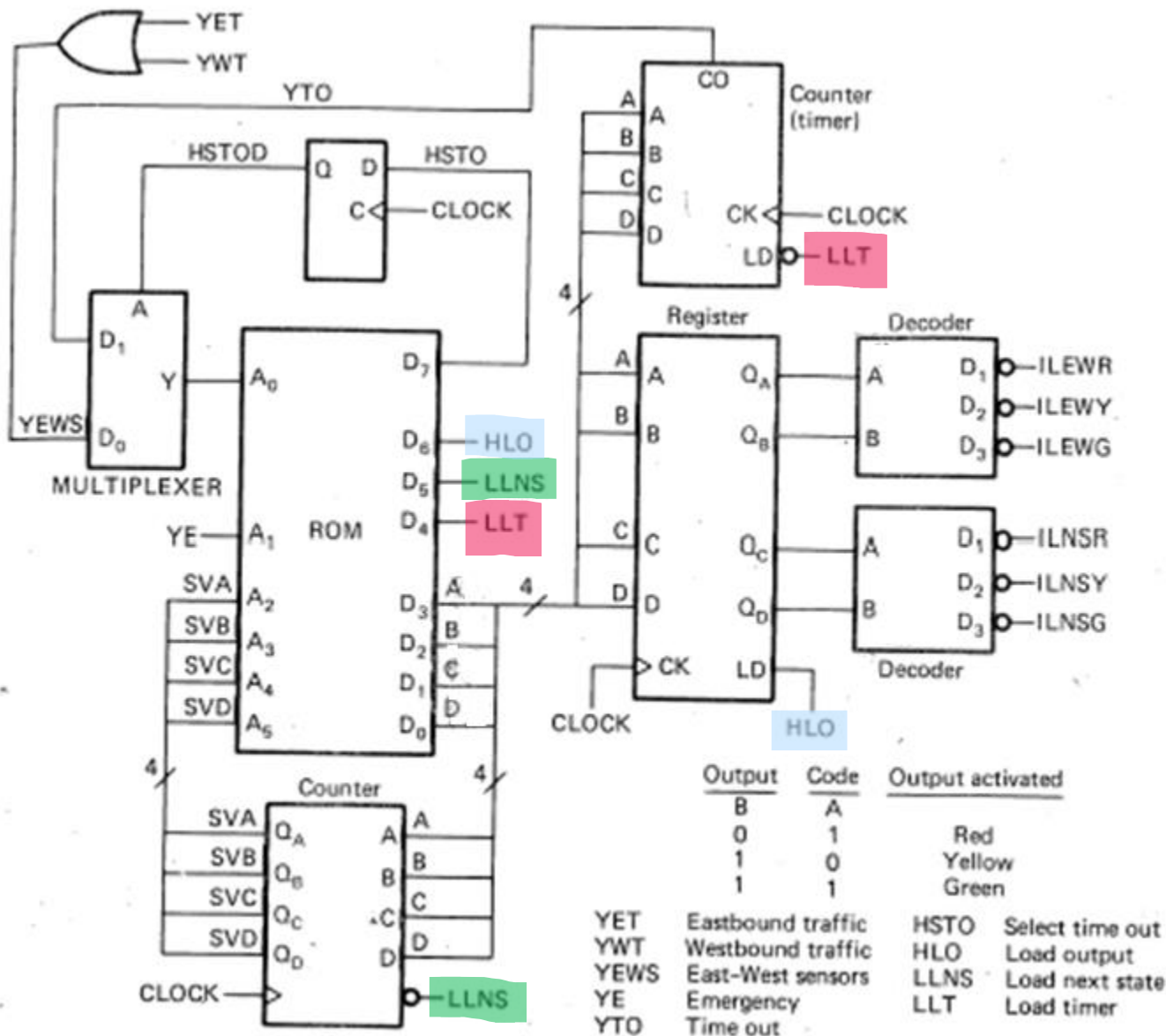


Figure 3-41 Traffic-light controller circuit.

1.25 s clock

# Traffic Light Controller Design Features

This design uses:

MUX inputs, and a direct input.

Decoders on the outputs.

A timer,

A state counter,

Registers on the outputs.

Does not show registers on the inputs (no need to take a “snapshot” of the lines as discussed previously.) However, all inputs are assumed to be synchronized with the clock (using a FF).

# “Traffic Light ASM from Hell”

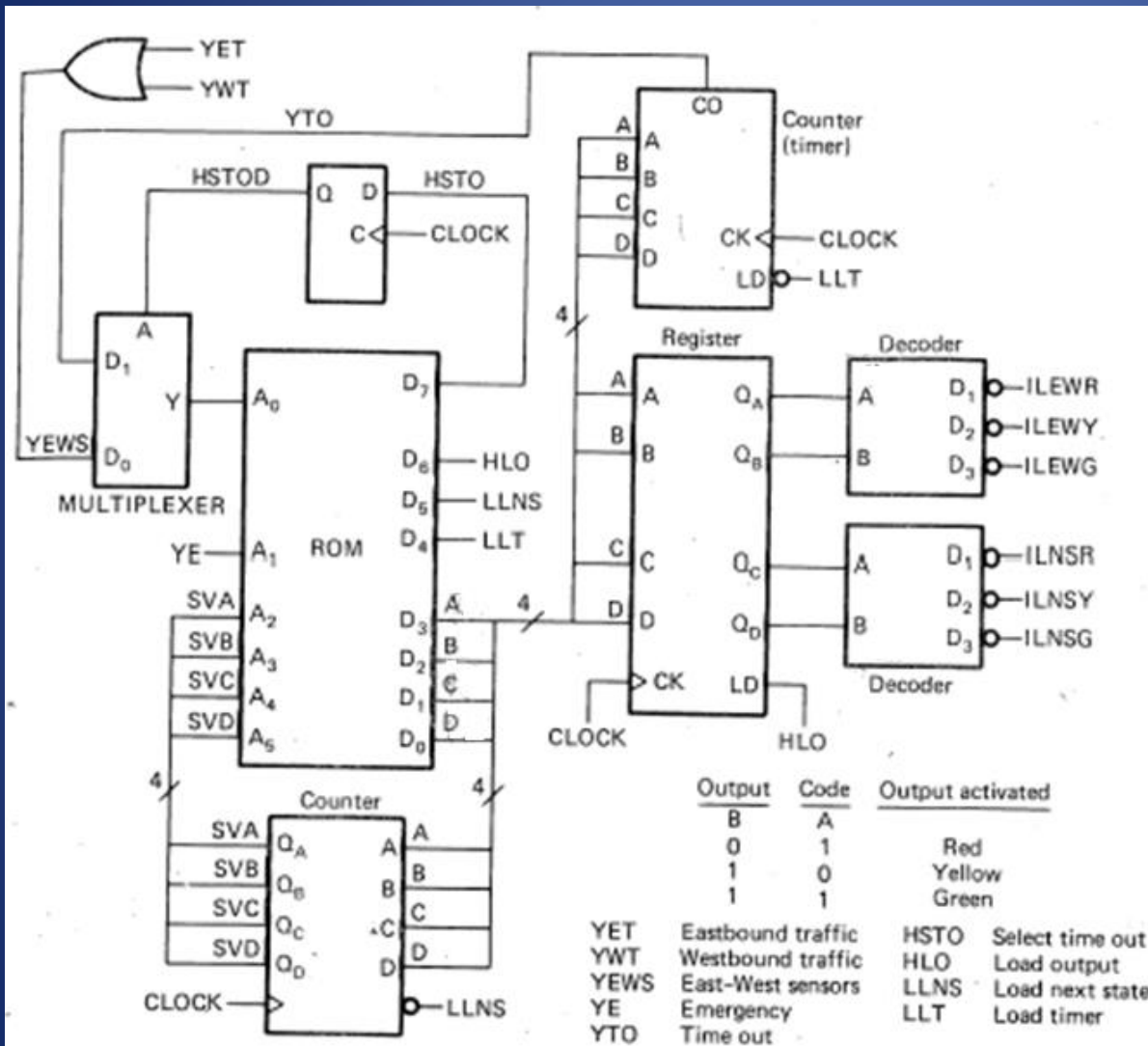



Figure 3-41 Traffic-light controller circuit.

NS is busy street.  
EW has traffic sensors.

Has emergency input.  
Goes to NSG/EWR  
when over.

Timer has adjustable  
delay times.

# Traffic Light Controller (cont'd)

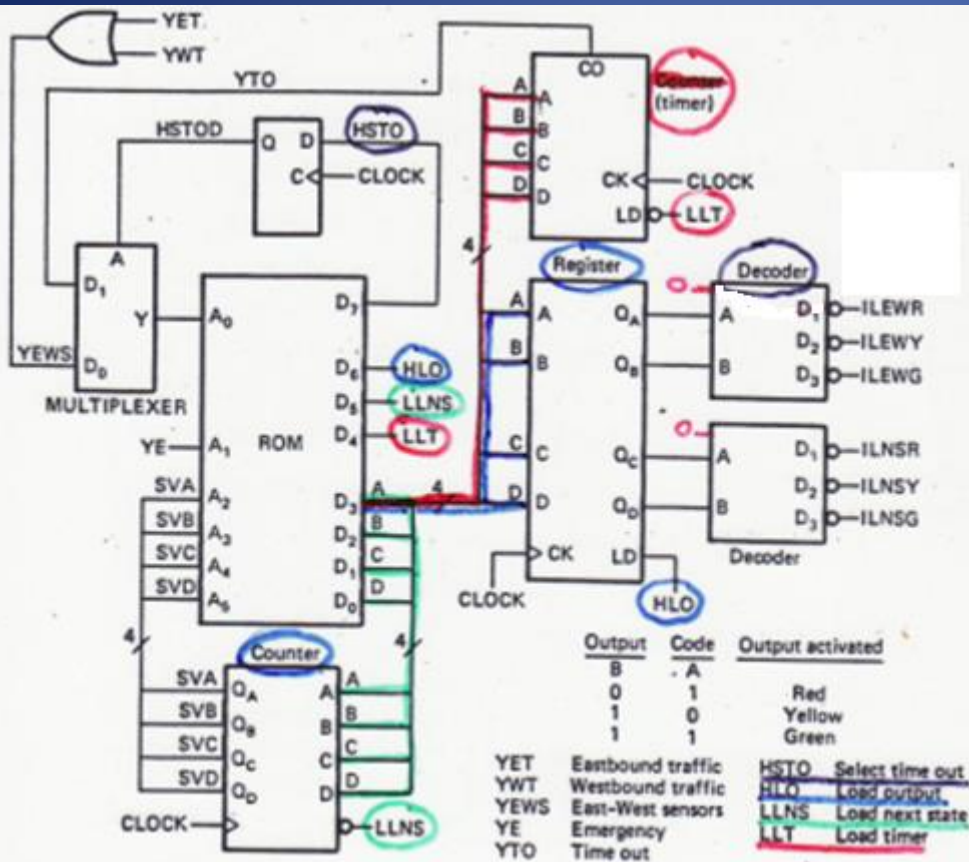

Data bus connected to state counter, timer, and output register. Load signals are: LLNS, LLT, and HLO.

So extra states will be needed to use the data bus for 3 things.

ASM chart branching by loading state counter.

E/W sensor (YEWS) and timer output (YTO) are multiplexed.  
 HSTO = 0 selects YEWS  
 HSTO = 1 selects YTO.

Active-low decoders allow 4 ROM outputs to control six lights.

Yemer is not multiplexed.



# More Traffic Light Controller Specs

East/West inputs are OR'ed together.

The MUX select line (HSTO) must be asserted early.

Note that LOAD's are color-coordinated in the previous figures.

Decoders are always enabled. (Notice the unused output D0 on the decoders.)

Uses 1.25 second clock: 16 states = 20 s; 4 states = 5 s

Register stores both decoder's binary select values.

# Traffic Light Controller ASM Chart


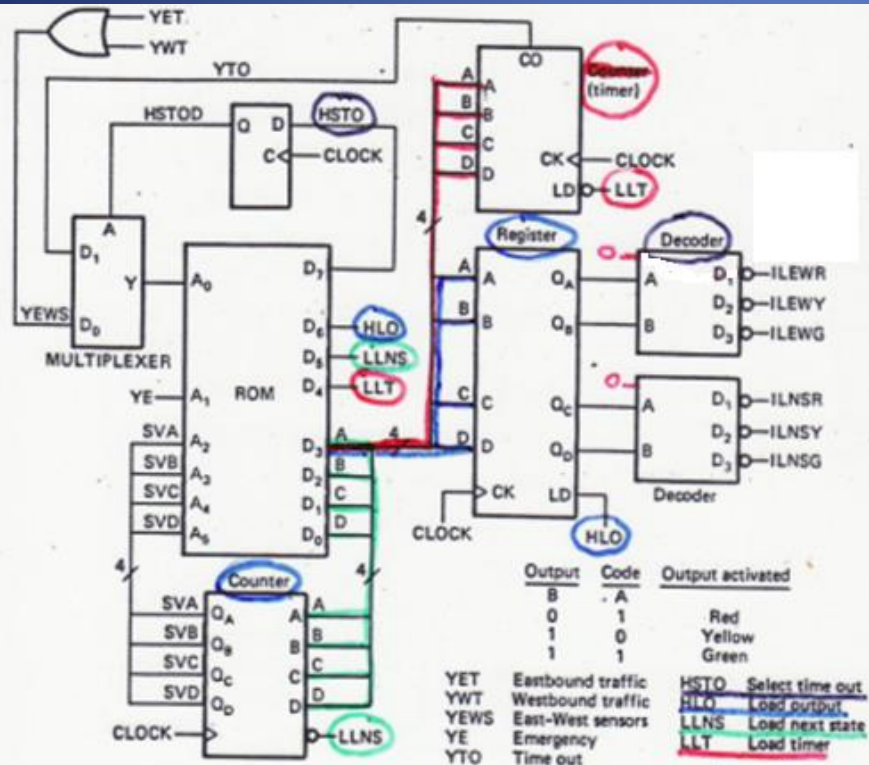


Figure 3-41 Traffic-light controller circuit.

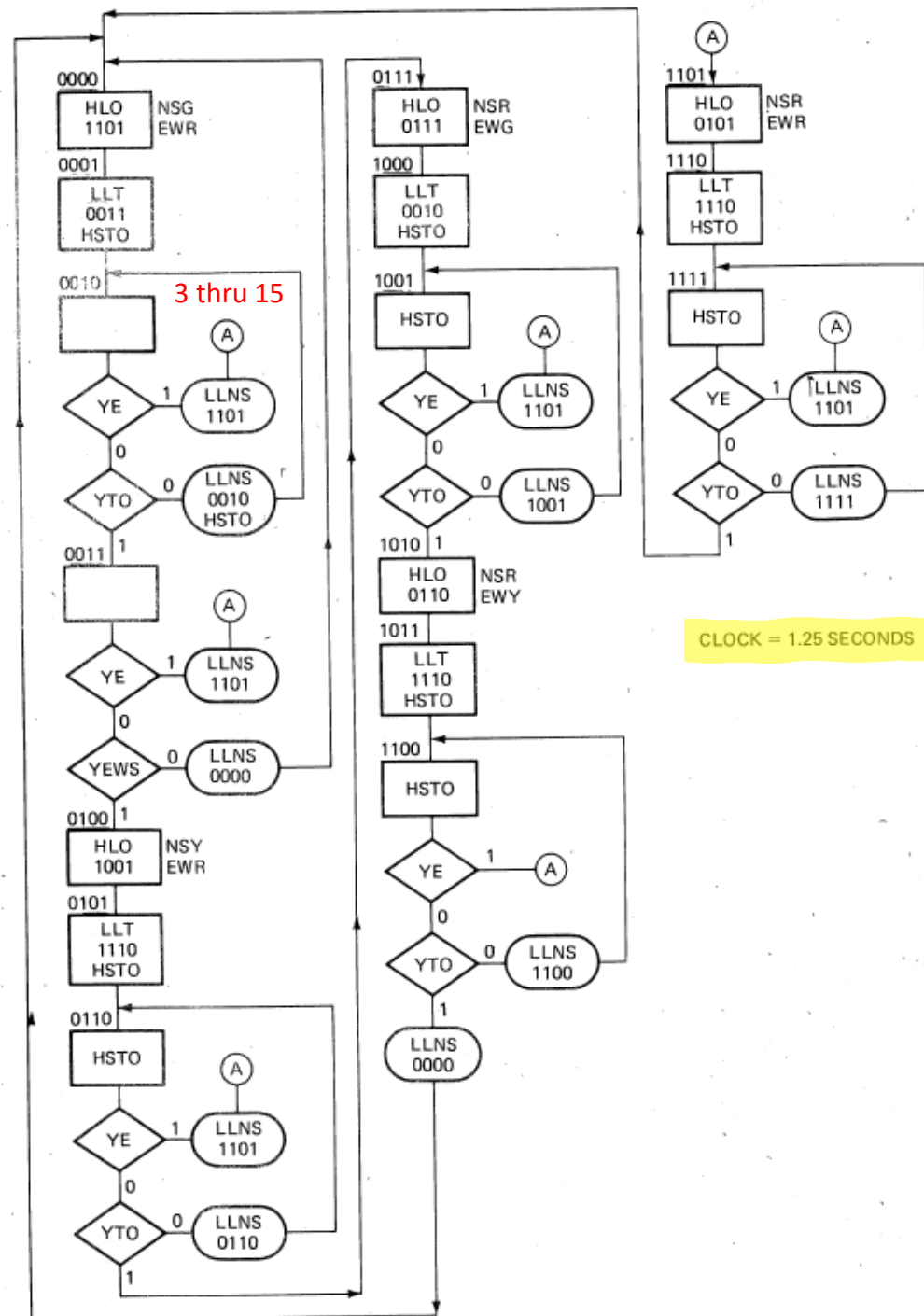



# Traffic Light Controller ROM Table

Table 3-5 Traffic light control ROM contents

Current state				YEWS									
A <sub>5</sub>	A <sub>4</sub>	A <sub>3</sub>	A <sub>2</sub>	YE	YTO	HSTO	HLO	LLNS	LLT	D	C	B	A
A <sub>5</sub>	A <sub>4</sub>	A <sub>3</sub>	A <sub>2</sub>	A <sub>1</sub>	A <sub>0</sub>	D <sub>7</sub>	D <sub>6</sub>	D <sub>5</sub>	D <sub>4</sub>	D <sub>3</sub>	D <sub>2</sub>	D <sub>1</sub>	D <sub>0</sub>
0	0	0	0	X	X	0	1	1	1	1	1	0	1
0	0	0	1	X	X	1	0	1	0	0	0	1	1
0	0	1	0	1	X	0	0	0	1	1	1	0	1
0	0	1	0	0	0	1	0	0	1	0	0	1	0
0	0	1	0	0	1	0	0	1	1	X	X	X	X
0	0	1	1	1	X	0	0	0	1	1	1	0	1
0	0	1	1	0	0	0	0	0	1	0	0	0	0
0	0	1	1	0	1	0	0	1	1	X	X	X	X
0	1	0	0	X	X	0	1	1	1	1	0	0	1
0	1	0	1	X	X	1	0	1	0	1	1	1	0
0	1	1	0	1	X	1	0	0	1	1	1	0	1
0	1	1	0	0	0	1	0	0	1	0	1	1	0
0	1	1	0	0	1	1	0	1	1	X	X	X	X
0	1	1	1	X	X	0	1	1	1	0	1	1	1
1	0	0	0	X	X	1	0	1	0	0	0	1	0
1	0	0	1	1	X	1	0	0	1	1	1	0	1
1	0	0	1	0	0	1	0	0	1	1	0	0	1
1	0	0	1	0	1	1	0	1	1	X	X	X	X
1	0	1	0	X	X	0	1	1	1	0	1	1	0
1	0	1	1	X	X	1	0	1	0	1	1	1	0
1	1	0	0	1	X	1	0	1	1	X	X	X	X
1	1	0	0	0	0	1	0	0	1	1	1	0	0
1	1	0	0	0	1	1	0	0	1	0	0	0	0
1	1	0	1	X	X	0	1	1	1	0	1	0	1
1	1	1	0	X	X	1	0	1	0	1	1	1	0
1	1	1	1	1	X	1	0	0	1	1	1	0	1
1	1	1	1	0	0	1	0	0	1	1	1	1	1
1	1	1	1	0	1	1	0	1	1	X	X	X	X